


# xor tb

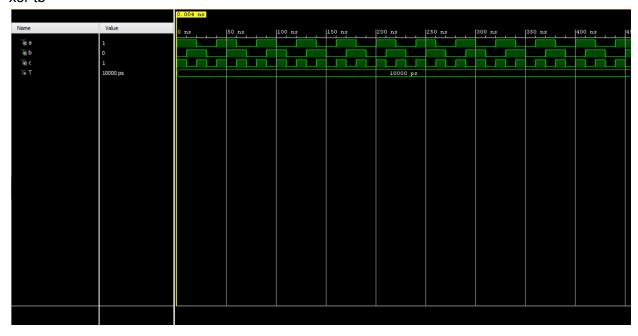


# D\_flip\_flop

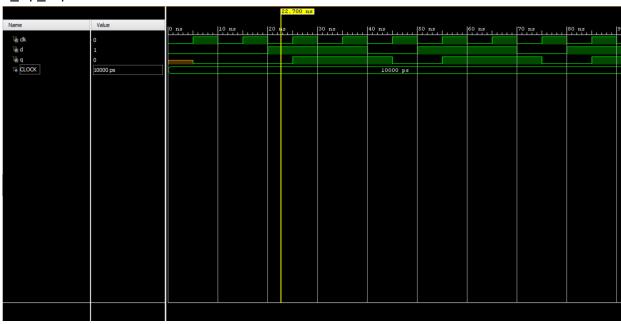


reg8

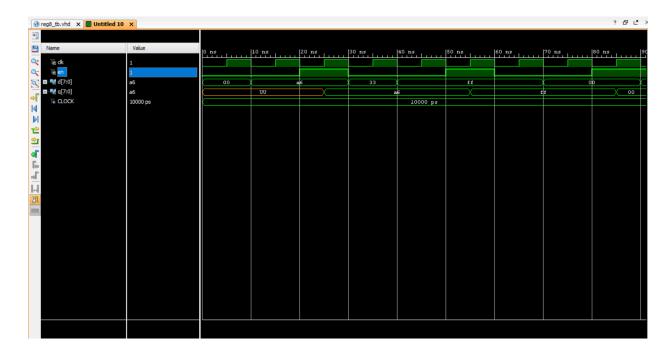


### shifter

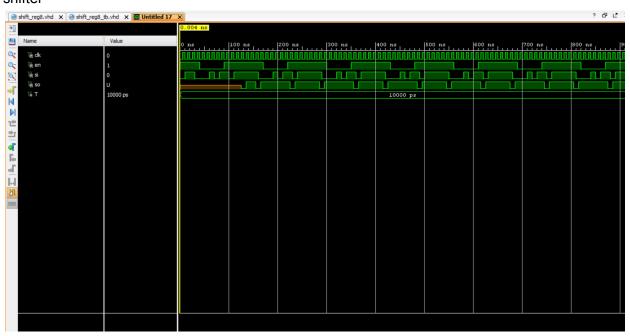


counter

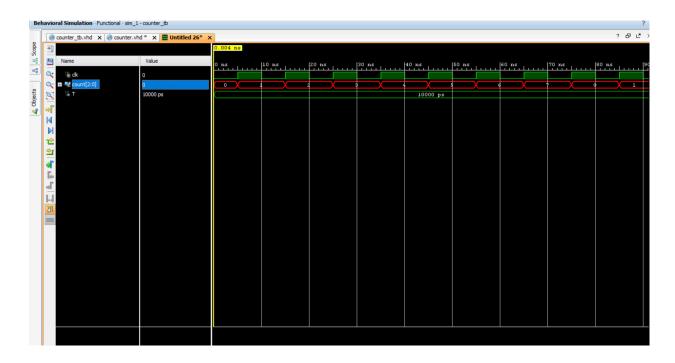

#### mux 4:1

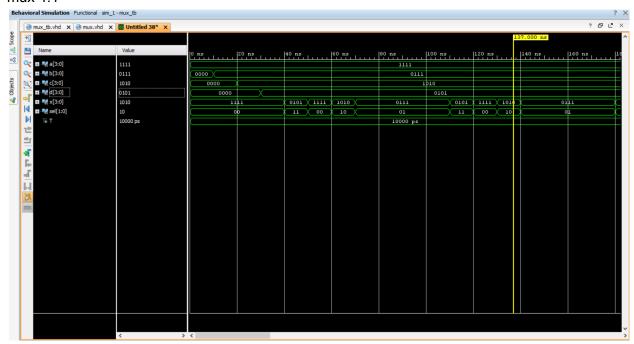

decoder

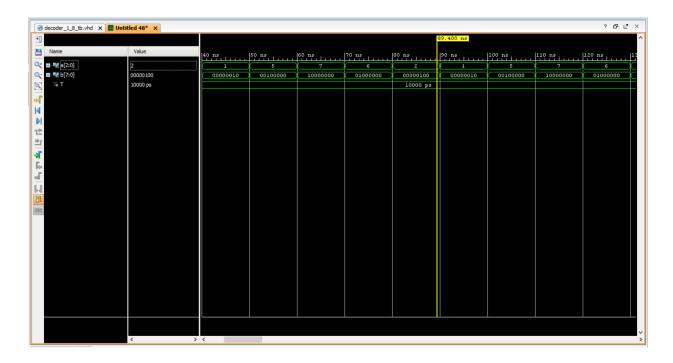

### bcd decoder ssd



demux 8bit 4:1